

Combinational circuits

Last time:

- Boolean functions e.g. $f(a,b,c) = ab + a\bar{c} + \bar{b}c$


truth table:

| a | b | c | ab | $a\bar{c}$ | $\bar{b}c$ | f |
|---|---|---|----|------------|------------|---|
| 0 | 0 | 0 | | | | |
| 0 | 0 | 1 | | | | |
| 0 | 1 | 0 | | | | |
| 0 | 1 | 1 | | | | |
| 1 | 0 | 0 | | | | |
| 1 | 0 | 1 | | | | |
| 1 | 1 | 0 | | | | |
| 1 | 1 | 1 | | | | |

fill in as exercise

- Logic gates e.g. AND, OR, NOT, XOR, NAND, ...

- Boolean functions as circuits

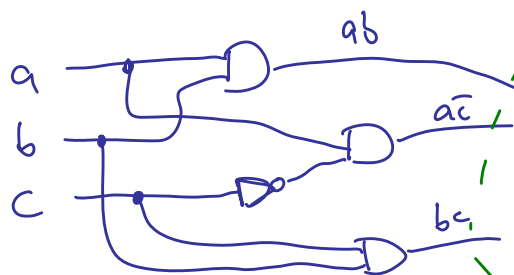

$f(a,b,c)$

complete as an exercise


Demo: TruthTable.java
with $a + \bar{b} + \bar{c}$

Today: Combinational circuits

- they produce outputs (almost instantaneously) from present inputs (do not depend on past inputs)
- any boolean function can be implemented as a combinational circuit
- every combinational circuit computes a boolean function.
- we study specific, useful circuits:
 - ① half adder
 - ② full adder
 - ③ decoder
 - ④ multiplexer

① Half adder

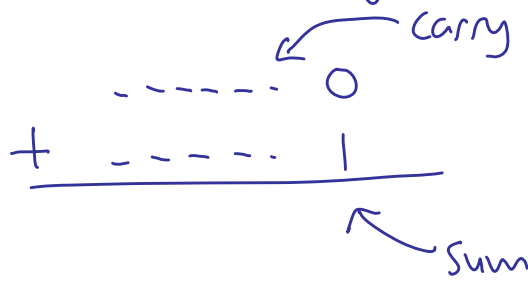
motivation: computes last digit of binary add



| Inputs | | Outputs | |
|--------|---|---------|-------|
| X | Y | Sum | Carry |
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |


↑
single gate?
XOR

↑
single gate?
AND

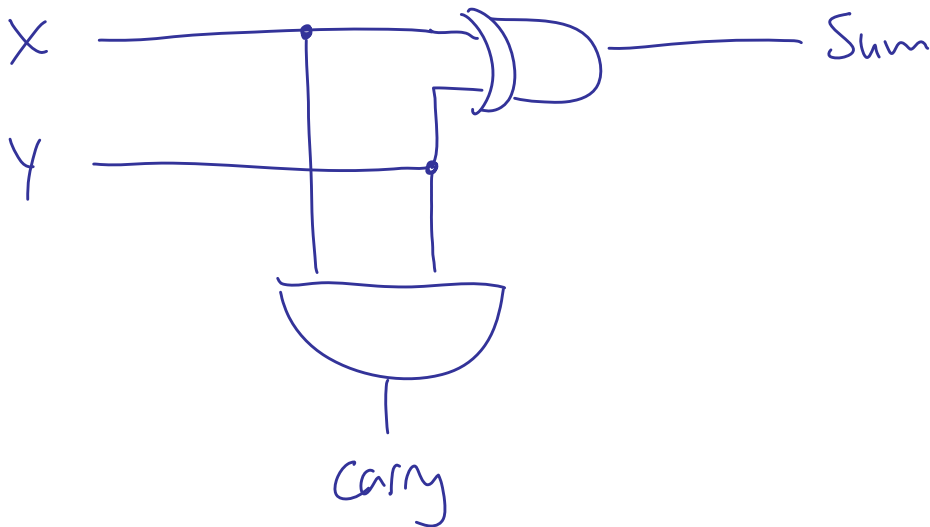


(2) Full adder

motivation: middle digit of binary add

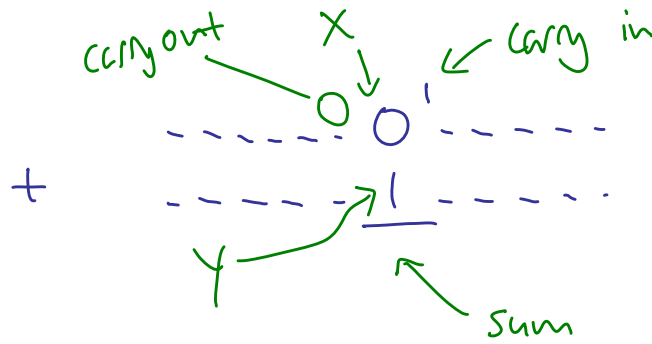

| Inputs | | | Outputs | |
|--------|---|----------|---------|-----------|
| X | Y | Carry In | Sum | Carry out |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

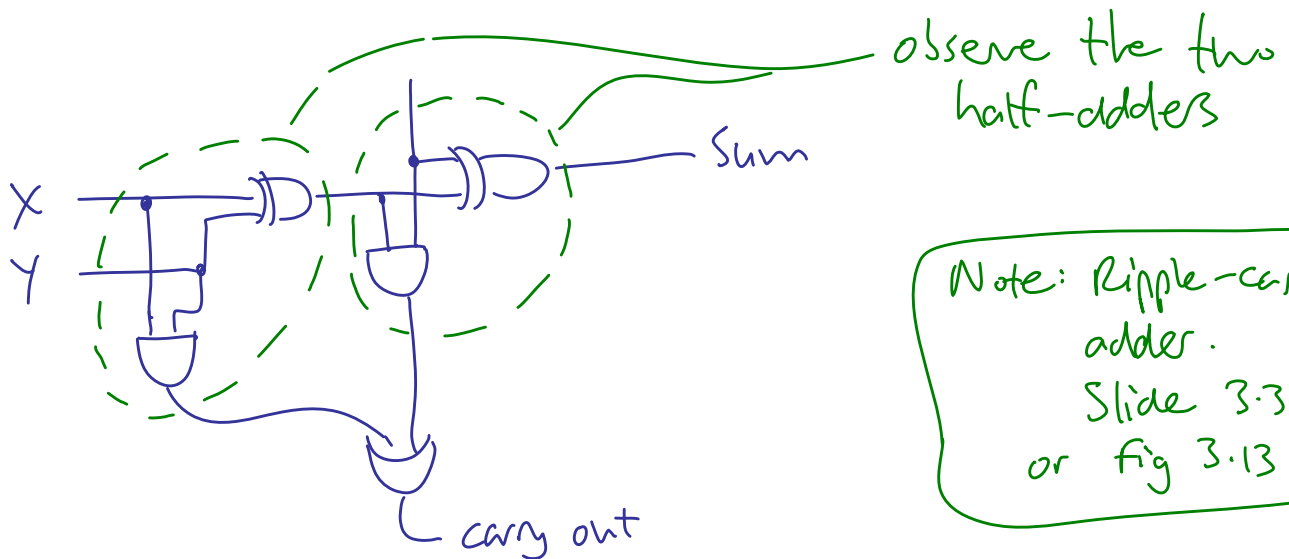


Note: Ripple-carry
adder.
Slide 3.35
or fig 3.13

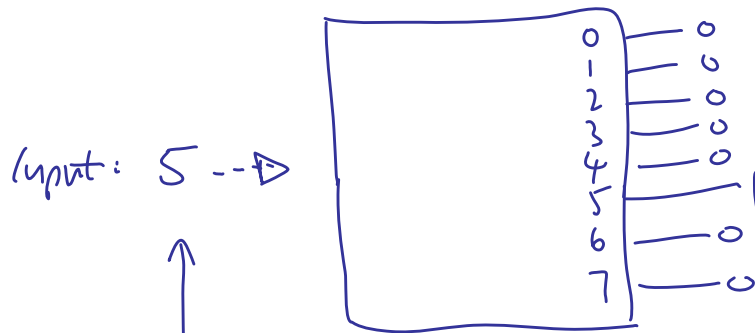(3) Decoder

- Input describes a number in some range, eg. $n \in \{0, 1, 2, \dots, 63\}$
- Output has one line for each possible input
- When input is n , the n th output line is on, all others are off


Motivation: Useful for activating a memory location based on its numerical address



how to describe this input?

Represent n as unsigned int. Need 3 input lines

eg. $n=6$

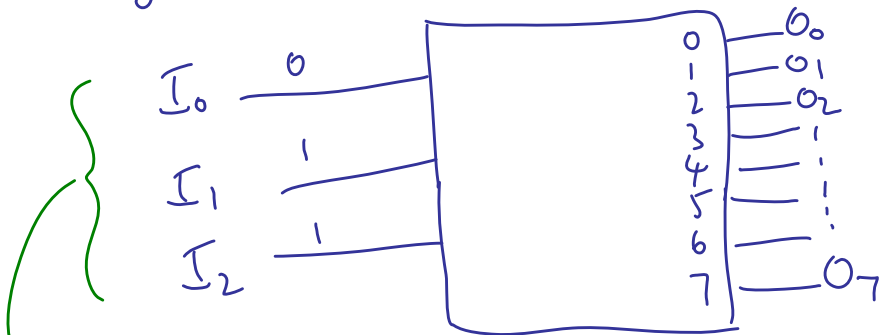


Note ordering of bits and interpretation. See fig 3.15 in textbook

Activity: Solve decoder puzzle on resources page.

ACTIVITY: create a 1-to-2 decoder

Answer:

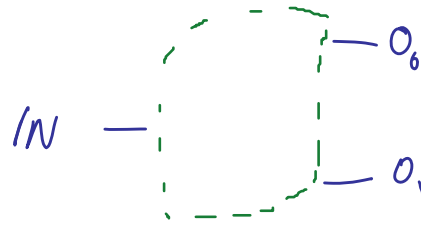


(Fill in missing part)

④ Multiplexer

- control lines specify a number in some range
e.g. $n \in \{0, 1, \dots, 3\}$
- input has one line for each control value.
- the single output is a copy of the n th input

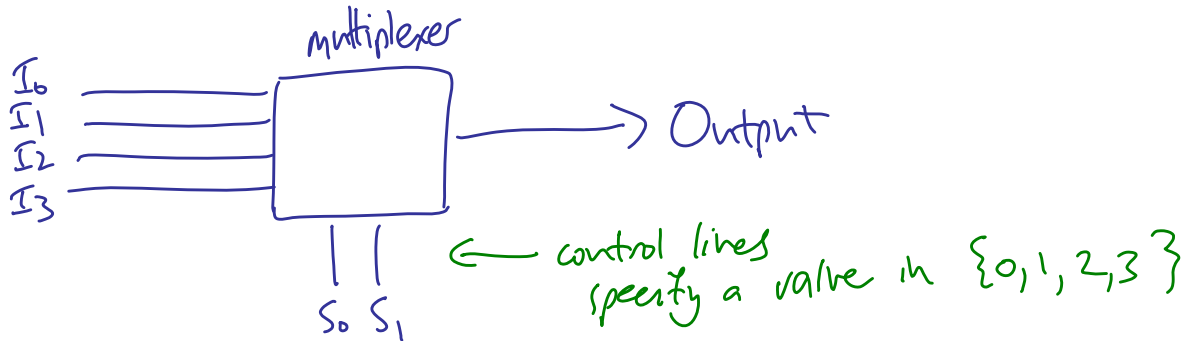useful for e.g. selecting a desired input on a data projector.



Activity: solve the multiplexer puzzle on resources page

See also: bit shifter circuit (consult text book & puzzles handout)

Objective is to shift the input left or right

e.g. 1101 shifted left is 1010 (fill in with 0)
shifted right is 0110 (fill in with 0)

Activity: create a 2-to-1 multiplexer in SimCir.

Solution: l_0 — — — — — output
 l_1 — — — — —

S_0 — — — — — (fill in missing part)

Challenge: Build a ripple carry adder for 4-bit addition.

Also, see online demos on resources page.